 



1 Decoders :-

The decoder is a combinational circuit that converts binary information from n input lines to a maximum of 2^n unique output lines. The decoders here are called n -to- m line decoders where $m \leq 2^n$.

3 to 8 line decoder -



Block Diagram

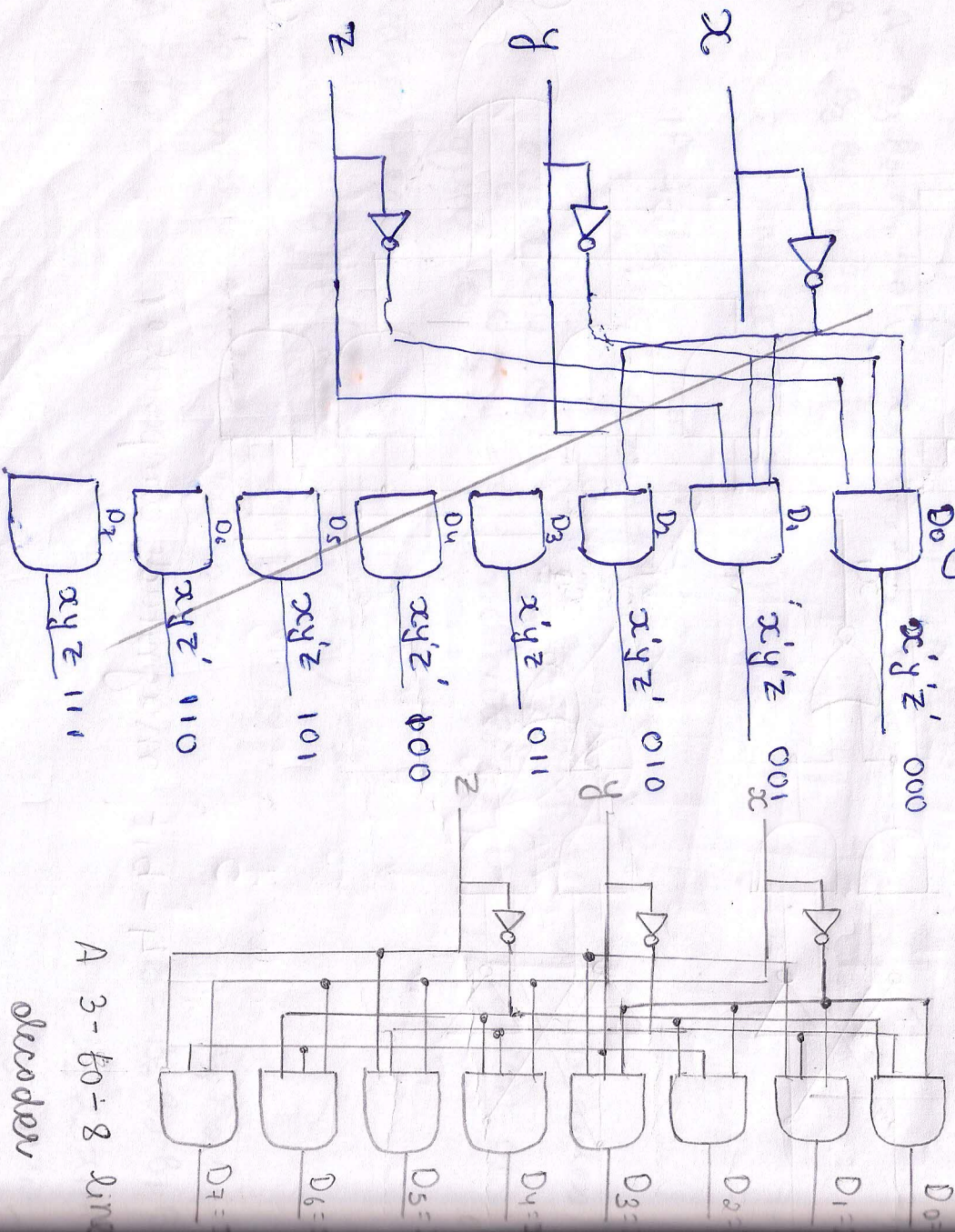

A 3-to-8 line decoder


Que:- Implement a full adder circuit with a decoder and two OR gates

$$S = x \oplus y \oplus z$$

$$C = xy + yz + xz$$


$$= x'y'z + x'yz' + xy'z + xyz$$

$$= x'yz + xy'z + xyz' + xyz$$

 

$$S = x \oplus y \oplus z = \sum (1, 2, 3, 7)$$

$$C = xy + yz + xz = \sum (3, 5, 6, 7)$$

 


Implementation of a full-adder with a decoder

De-Multiplexer (demux) :-

Decoders include one or more enable inputs to control the circuit operation.

2 to 4 decoder with enable input.

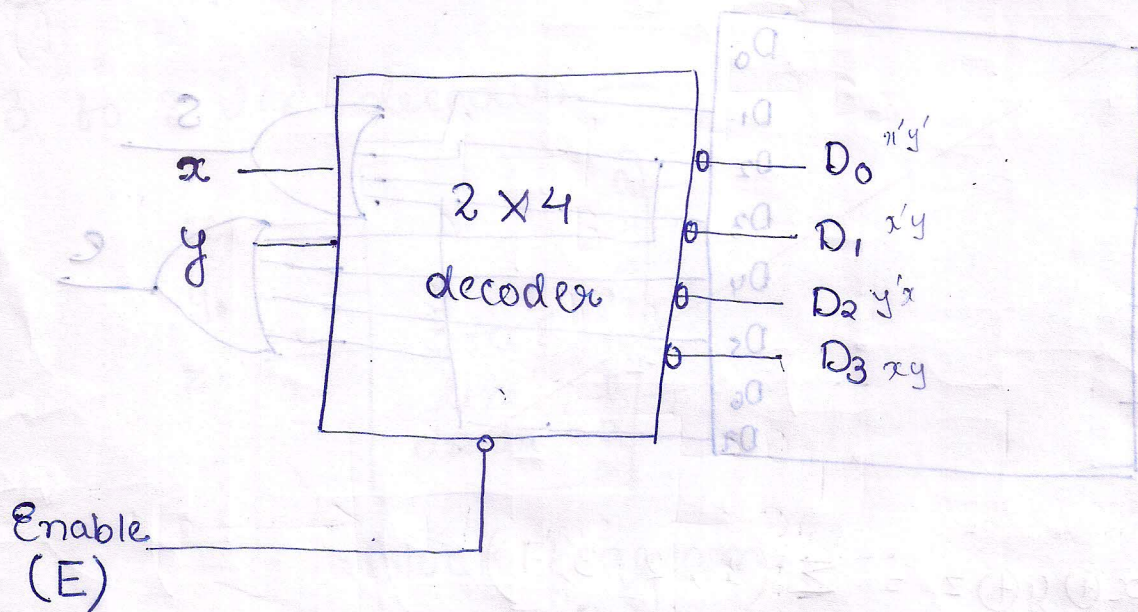


Here all the outputs are equal to 1 if enable input is 1, regardless of the values of inputs x and y . When the enable input is 0, the circuit operates as a decoder with complemented outputs.

x	y	E	D_0	D_1	D_2	D_3
0	0	0				
0	0	1	1	1	1	1
0	1	0				
0	1	1	1	1	1	1
1	0	0				
1	0	1	1	1	1	1
1	1	0				
1	1	1	1	1	1	1


E	X	Y	D ₀	D ₁	D ₂	D ₃
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

xy
 $xy = 1$
 $D_0 = (xy)'$
 $D_1 = (x'y)'$
 $D_2 = (xy)'$
 $D_3 = (xy)'$

Circuit diagram

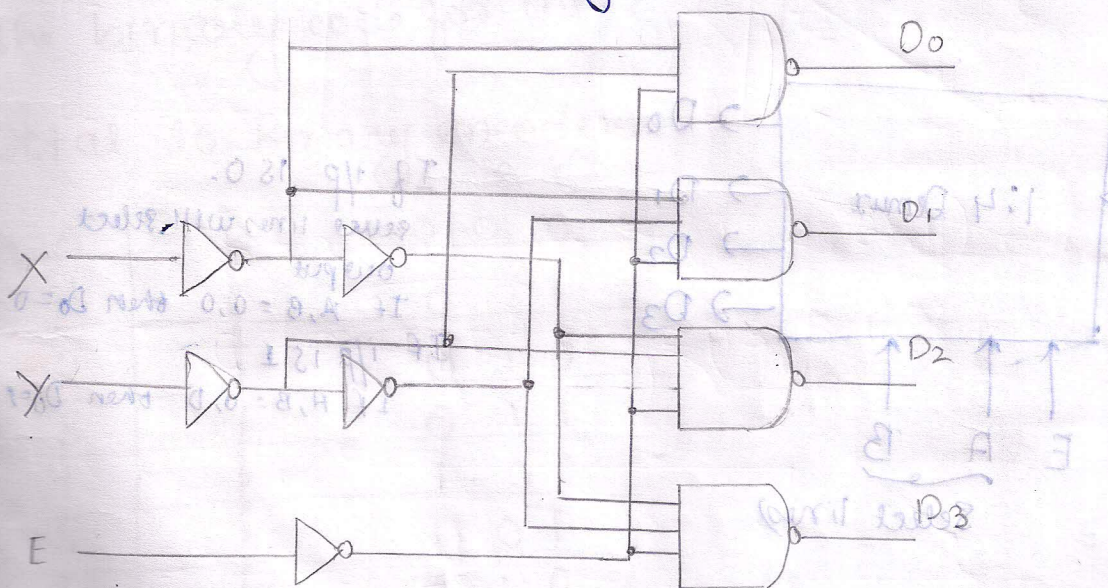

A 2-to-4 line decoder with enable input

 

A decoder with an enable input is a demultiplexer. A demultiplexer is a circuit that receives information on a single line and transmits this information on one of 2^n possible ^{output} lines. The selection of a specific output line is controlled by the bit values of n selection lines.