

24.04.2015

State Equation

1) State equation is an algebraic equation that specifies the conditions for a flipflop state transition.

2) The left side of the equation denotes the next state of a flipflop and the right side of a Boolean function that specifies the present state conditions that make the next state equal to 1.

3) From the next state columns, we note that the flipflop A goes to the 1's state four times i.e.:- when $x=0$ and $AB=01$ or 10 , or 11 and when $x=1$ and $AB=11$.

$$A(t+1) = (A'B + AB' + AB)x' + ABx$$

$$= x'A'B + x'AB' + x'AB + xAB$$

x \ AB	00	01	11	10
0				1
1	1		1	1

$= A'B + xA + xB'$
 $= AB' + x(A+B)$
 $= (A+B)x + A'B$

The right hand side of the state equation is a Boolean function for a present state.

When this function is equal to 1, the occurrence of a clock pulse causes flipflop A, to have a next state of '1'.

When this function is equal to 0, the occurrence of a clock pulse causes flipflop A, to have a next state of '0'.

On reducing the eqn -

$$x'(A+B) + AB$$

$$= Bx' + (B+x')A$$

$$= Bx' + (B'x)A$$

x \ AB	00	01	11	10
0		1	1	1
1			1	

$$= x'B + AB + x'A$$

If we let, $S = Bx'$ and $R = xB'$

Then eqn

$$A(t+1) = S + R'A$$

Now,

$$B(t+1) = (A'B)x' + (A'B' + A'B + AB)x$$

$$= x'A'B + xA'B' + xA'B + xAB$$

$$B(t+1) = A'B + x(A'+B)$$

$$= A'B + xA' + Bx$$

$$= A'x + B(x+A')$$

$$A'x + (xA')B$$

$x \backslash B$	00	01	11	10
0		1		
1	1	1	1	

$$= A'B + x(A'+B)$$

If we let

$S = xA'$ and $R = x'A$

then

$$B(t+1) = S + R'B$$

Flipflop Input Function :-


We shall adopt a convention of using two letters to designate a flipflop input variable. i.e.:- the first designates the name of the input and the second the name of the flipflop.

Eg:- $JA' = BC'x + B'Cx'$

$$KA = B + y$$

Here JA and KA denotes two Boolean variables. The first letter denote J and K input respectively of a JK flipflop.

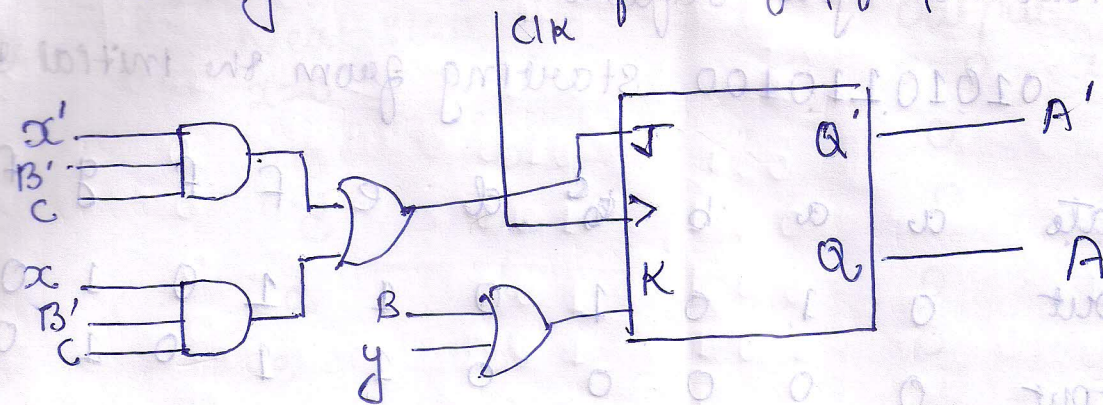Second letter is the symbol name of the flipflop.



For the example considered, input function can be written as —

$$SA = x'B$$

$$RA = xB'$$

$$y = xAB'$$

$$SB = xA'$$

$$RB = x'A$$

State Reduction and Assignment :-

State Reduction :-

The reduction of the number of flipflops in a sequential circuit is referred to as the state reduction problem.

