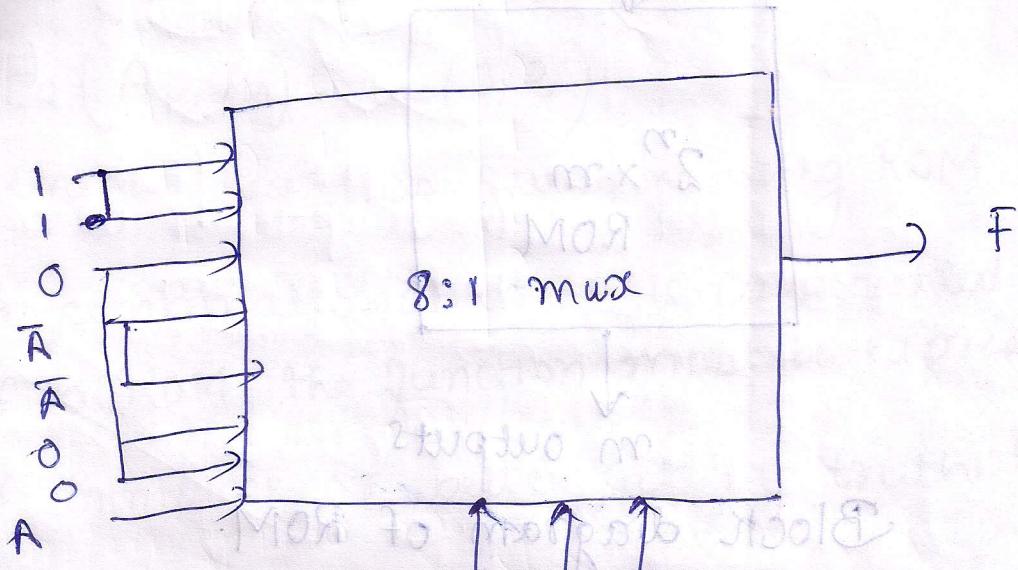



	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
\bar{A}	①	②	2	③	④	5	6	7
A	⑧	⑨	10	11	12	13	14	⑮



• Will take one bit from each of the 8 inputs + It


• will add all address bits to select the required output
(Combine common inputs)

Symbol of MUX

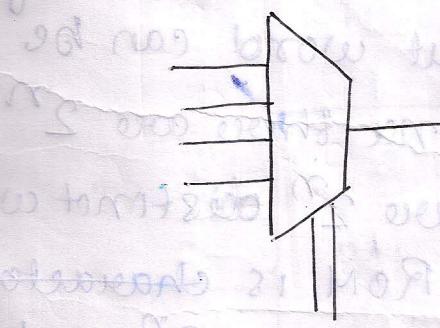

READ ONLY MEMORY:- ROM

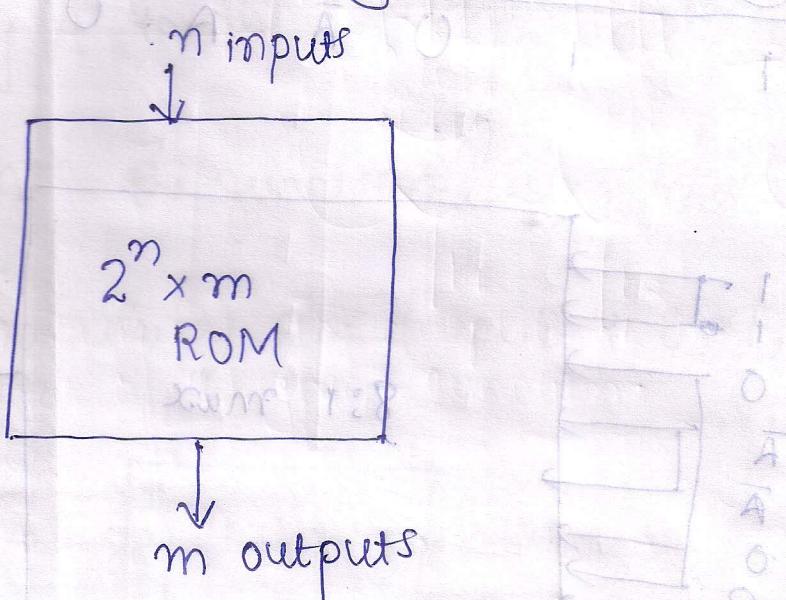A ROM is a device that includes both the decoder and 'OR' GATES within a single IC package.



Block diagram of ROM

It consists of n input lines and m output lines. Each bit combination of the input variables is called an address. Each bit combination that comes out of the output lines is called a word. The number of bits per word is equal to the no. of output lines m . An address is essentially a binary number that denotes one of the minterms of n variable. An output word can be selected by a unique address and since there are 2^n distinct addresses in a ROM, there are 2^n distinct words which can be stored in the unit. A ROM is characterised by the number of words, i.e. 2^n and number of bits per word m .

Eg:- 32 X 8 ROM

$2^5 \times 8$
 \downarrow
 \downarrow
5:32 decoder
8 OR Gates

Ques:- $F_1(A_1, A_0) = \sum(1, 2, 3)$


$F_2(A_1, A_0) = \sum(0, 2)$


Implement these two functions using ROM

⇒ When a combinational circuit is implemented by means of a ROM, the function must be expressed in SUM of minterms or better yet by truth table

Truth Table

A_1	A_0	F_1	F_2
0	0	0	1
0	1	1	0
1	0	1	1
1	1	1	0

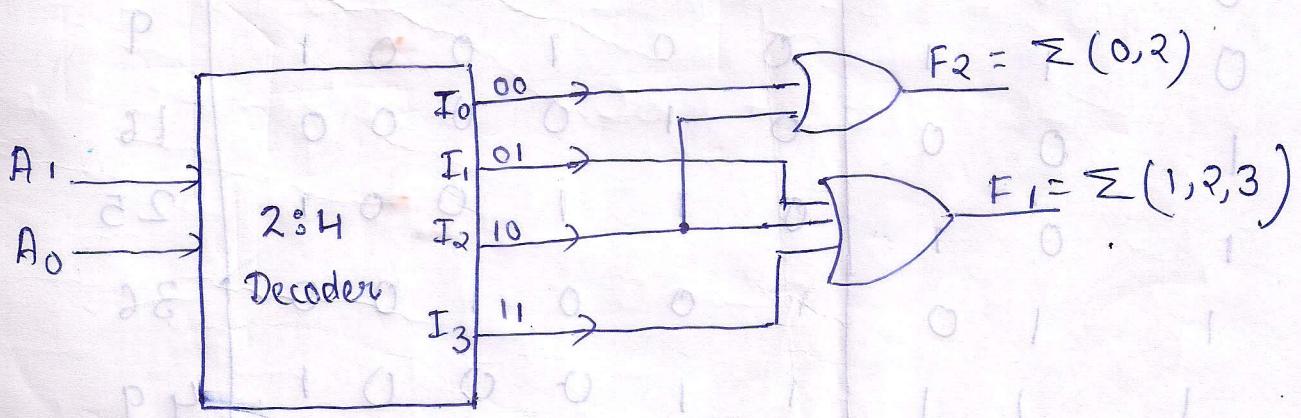

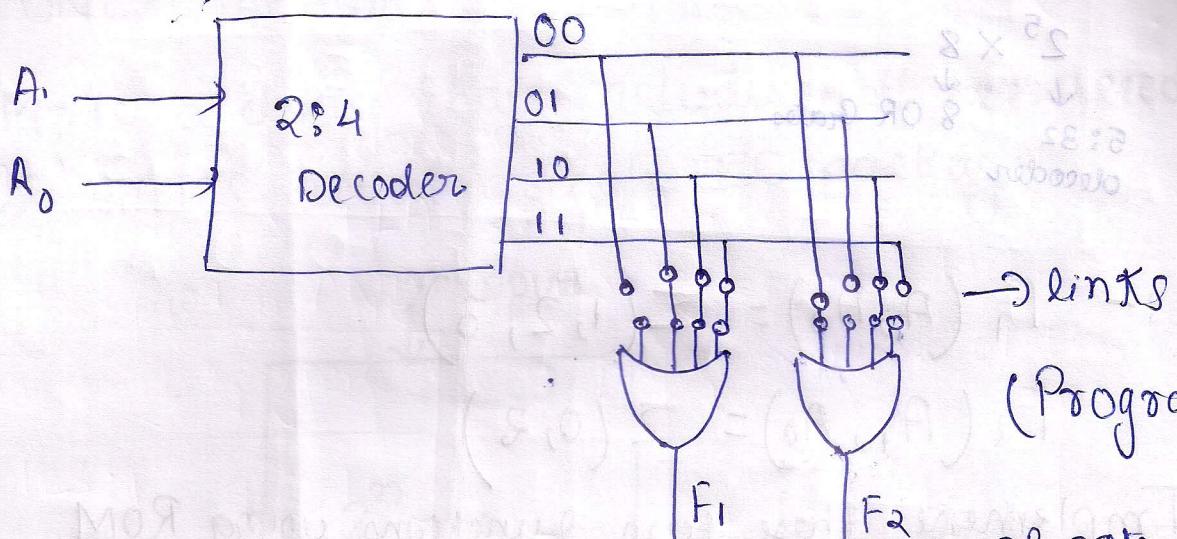


If there is inverter at the output of the OR gate then link the complement of the given function.
 Design a combinational circuit using a ROM.
 The circuit accepts a 3 bit number and generates a
 output binary number equal to square of its number.

Truth Table

A_2	A_1	A_0	B_5	B_4	B_3	B_2	B_1	B_0	Decimal
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

$\therefore B_1 = 0$ (always) and $B_0 = A_0$ (implied)
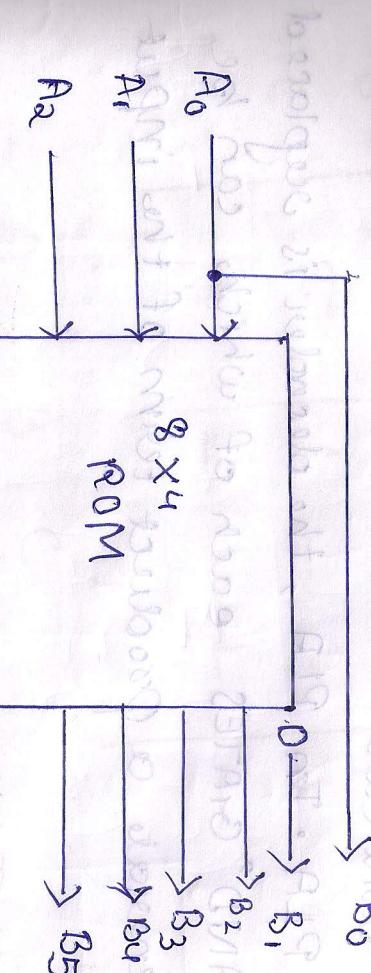
$$\therefore \text{ROM required} \approx 2^3 \times 4 = 8 \times 4$$



ROM Truth Table

A ₂	A ₁	A ₀	B ₅	B ₄	B ₃	B ₂
0	0	0	0	0	0	0
0	0	1	-	-	-	-
0	1	0	-	-	-	-
0	1	1	0	0	0	0
1	0	0	0	0	0	0
1	0	1	-	0	0	0
1	1	0	0	0	0	0
1	1	1	-	-	-	-

$$J'A + JA = J'A + J'A = 0$$

$$JA + 'JA = JA + 'JA = 0$$

$$J'A + JA = J'A + 'JA = 0$$

$$JA + 'JA = JA + 'JA = 0$$

$$B_0 = A_0$$

$$B_1 = 0$$

$$B_2 = 0$$

$$B_3 = 0$$

$$2^{(2^3-1)} = 8$$

$$2^{(2^3-1)} = 8$$

$$2^{(2^3-1)} = 8$$

$$2^{(2^3-1)} = 8$$